

# Computação Reconfigurável

## Aula 2

Valeri Skliarov, Prof. Catedrático

Email: [skl@ua.pt](mailto:skl@ua.pt)




URL: <http://sweet.ua.pt/skl/>

Departamento de Eletrónica, Telecomunicações e Informática  
Universidade de Aveiro

<http://elearning.ua.pt/>

# Revisão da aula anterior

## Primeiros passos:

   

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TopTrivial is
    port (    sw    : in std_logic_vector (15 downto 0);
           led     : out std_logic_vector (15 downto 0));
end TopTrivial;

architecture Behavioral of TopTrivial is
begin
    led <= sw;
end Behavioral;
```

```
# Switches
#Bank = 34, Pin name = IO_L21P_T3_DQS_34, Sch name = SW0
set_property PACKAGE_PIN U9 [get_ports {sw[0]]}

set_property IOSTANDARD LVCMOS33 [get_ports {sw[0]]}
#Bank = 34, Pin name = IO_25_34,Sch name = SW1
set_property PACKAGE_PIN U8 [get_ports {sw[1]]}

set_property IOSTANDARD LVCMOS33 [get_ports {sw[1]]}
#Bank = 34, Pin name = IO_L23P_T3_34,Sch name = SW2
set_property PACKAGE_PIN R7 [get_ports {sw[2]]}

set_property IOSTANDARD LVCMOS33 [get_ports {sw[2]]}
#Bank = 34, Pin name = IO_L19P_T3_34,Sch name = SW3
set_property PACKAGE_PIN R6 [get_ports {sw[3]]}

set_property IOSTANDARD LVCMOS33 [get_ports {sw[3]]}
#Bank = 34, Pin name = IO_L19N_T3_VREF_34,Sch name = SW4
set_property PACKAGE_PIN R5 [get_ports {sw[4]]}

set_property IOSTANDARD LVCMOS33 [get_ports {sw[4]]}
#Bank = 34, Pin name = IO_L20P_T3_34,Sch name = SW5
set_property PACKAGE_PIN V7 [get_ports {sw[5]]}

set_property IOSTANDARD LVCMOS33 [get_ports {sw[5]]}
#Bank = 34, Pin name = IO_L20N_T3_34,Sch name = SW6
set_property PACKAGE_PIN V6 [get_ports {sw[6]]}

set_property IOSTANDARD LVCMOS33 [get_ports {sw[6]]}
#Bank = 34, Pin name = IO_L10P_T1_34,Sch name = SW7
set_property PACKAGE_PIN V5 [get_ports {sw[7]]}
```

# Aula 2

- Síntese e simulação
- Tipos de dados, objetos e operadores
- Instruções de controlo – decisão: *if, when, with, case*
- Processos combinatórios e sequenciais
- VHDL comportamental e estrutural
- Exemplos:
  - Operações aritméticas
  - Processos
  - Conversão de tipos

Bibliografia: V.Sklyarov, I.Skliarova, A.Barkalov, L.Titarenko. Synthesis and Optimization of FPGA-Based Systems. Springer, 2014.

# VHDL (três partes principais)

## Três partes principais:

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;
```

Incluir bibliotecas necessárias

```
entity TopTrivial is  
    port (    sw    : in std_logic_vector (15 downto 0);  
           led     : out std_logic_vector (15 downto 0));  
end TopTrivial;
```

Declarar entidade

```
architecture Behavioral of TopTrivial is  
begin  
    led <= sw;  
end Behavioral;
```


Descrever arquitetura

## Bibliotecas mais comuns:

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
use IEEE.STD_LOGIC_ARITH.all;  
use IEEE.STD_LOGIC_UNSIGNED.all;
```

ou
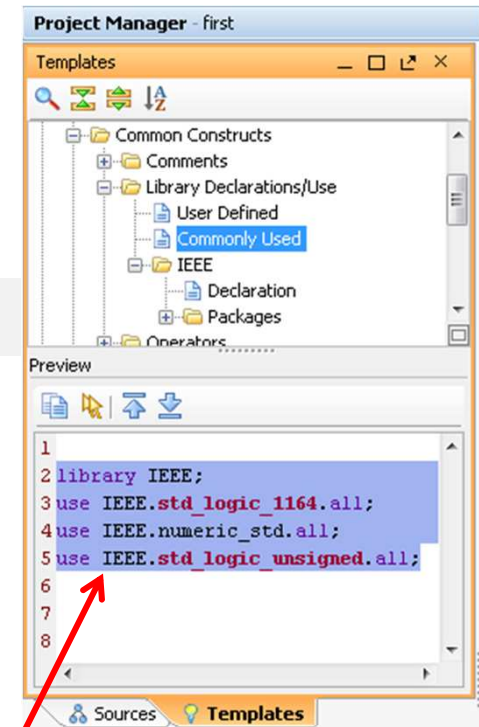
```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.numeric_std.all;  
use IEEE.std_logic_unsigned.all;
```



# VHDL (três tipos de descrição principais)

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity TopTrivialNew is
    port (    clk      : in std_logic;
            sw       : in std_logic_vector (15 downto 0);
            led      : out std_logic_vector (15 downto 0));
end TopTrivialNew;

architecture my of TopTrivialNew is

    signal    divided_clk      : std_logic;

begin

    led <= sw when divided_clk = '1' else (others => '0');

    div      :      entity work.clock_divider
                port map( clk, '0', divided_clk);

end my;
```

VHDL:

1. Comportamental.
2. Estrutural.
3. Misto

Declaração de sinais

Frequência do relógio  
da placa **100 MHz**

# VHDL (sumário)

Declaração de bibliotecas  
**library** ...  
**use** ...

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
use IEEE.STD_LOGIC_ARITH.all;  
use IEEE.STD_LOGIC_UNSIGNED.all;
```


```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.numeric_std.all;  
use IEEE.std_logic_unsigned.all;
```

Descrição de entidade (interface)  
**entity** <nome de entidade> **is**  
Declaração de parâmetros genéricos – **generic**  
Declaração de portas – **port**  
**end** <nome de entidade>

parte  
declarativa  
de entidade

```
entity Counter is  
  generic (N : integer := 3);  
  port (  
    reset : in std_logic;  
    clk    : in std_logic;  
    My_count: out std_logic_vector(N downto 0)  
  );  
end Counter;
```

Descrição de arquitetura (funcionalidade)  
**architecture** <nome de arquitetura> **of** <nome de entidade> **is**  
Declaração de sinais– **signal**  
Declaração de constantes – **constant**  
Declaração de tipos– **type**  
Declaração de componentes– **component**  
Declaração de funções– **function**  
Declaração de procedimentos– **procedure**  
Declaração de variáveis partilhadas– **shared variable**  
**begin**  
Corpo de arquitetura  
**end** <nome de arquitetura>

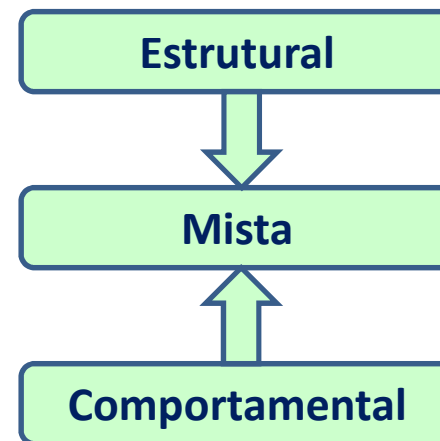

parte declarativa de arquitetura

The screenshot shows a code editor with Verilog code. A red arrow points to the first line of a process block, which is highlighted in blue. A context menu is open over the code, with the 'Toggle Line Comments' option highlighted in yellow. Below the code, there is a table with four columns: 'IS', 'TPWS', 'Failed Routes', and 'LUT'. The table contains two rows of data.

```
--process (sw)
--begin
--  case sw is
--    when "00" => led <= "0001";
--    when "01" => led <= "0010";
--    when "10" => led <=
--    when "11" => led <=
--    when others => led <=
--  end case;
--end process;
```

```
--process (sw)
--begin
--  if      sw = "00" then 1
--  elsif   sw = "01" then 1
--  elsif   sw = "10" then 1
--  elsif   sw = "11" then 1
--  else    led <= "0000";
--  end if;
--end process;
```

end Behavioral;

IS	TPWS	Failed Routes	LUT
0.00	0.00	0	0.01



-- comentários até final da linha

Inserir/remover  
comentários para  
um conjunto de  
linhas



# Síntese e simulação



**Simulação  
comportamental**

Geralmente vai precisar de duas partes:  
1) Código VHDL de que queremos simular;  
2) Código VHDL adicional que se chama *testbench*.

**Síntese,  
implementação  
e teste**

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
  
entity TopTrivial is  
    port (    sw    : in std_logic_vector (15 downto 0);  
           led     : out std_logic_vector (15 downto 0));  
end TopTrivial;  
  
architecture Behavioral of TopTrivial is  
begin  
    led <= sw;  
end Behavioral;
```

por exemplo:




# Simulação. Exemplo 1.

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity TopTrivial is
    port (    sw    : in std_logic_vector (15 downto 0);
           led     : out std_logic_vector (15 downto 0));
end TopTrivial;

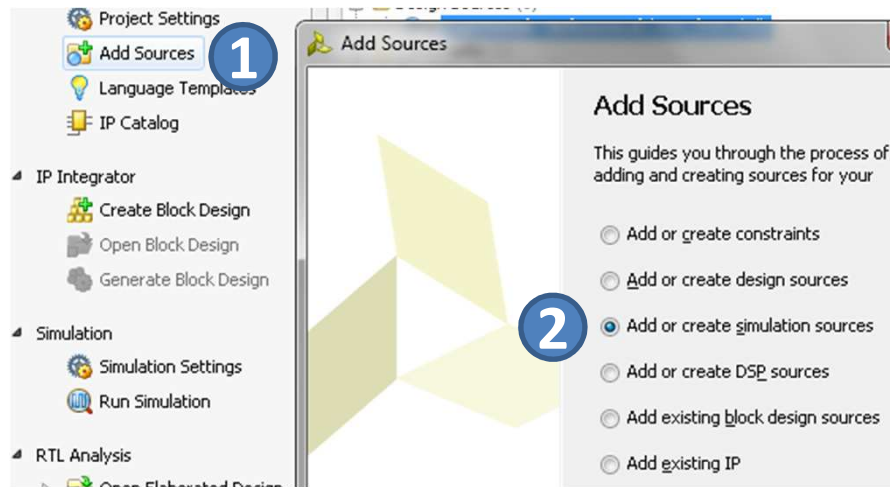architecture Behavioral of TopTrivial is
begin
    led <= sw;
end Behavioral;
```



```
library IEEE;
use IEEE.std_logic_1164.all;
entity for_example is
end for_example;
architecture behavior of for_example is
    signal sw_in    : std_logic_vector (15 downto 0);
    signal led_out   : std_logic_vector (15 downto 0);
    component TopTrivial
        port (    sw    : in STD_LOGIC_VECTOR (15
downto 0);
              led     : out STD_LOGIC_VECTOR (15
downto 0));
    end component;
begin
    uut: TopTrivial
    port map (sw => sw_in, led => led_out);
    stim_proc: process
    begin
        sw_in <= (others => '1');
        wait for 50 ns;
        sw_in <= (others => '1');
        wait for 100 ns;
        sw_in <= (15 downto 10 => '1', others => '0');
        wait for 50 ns;
        sw_in <= "1010101010101010";
        wait for 70 ns;
        sw_in <= (15 downto 13 => '1', 10 => '1', 6 downto 5
=> '1', others => '0');
    end process;
end behavior;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity TopTrivial is
```


```
library IEEE;
use IEEE.std_logic_1164.all;
entity for_example is
end for_example;
```



## Testbench


```
of for_example is
d_logic_vector (15 downto 0);
d_logic_vector (15 downto 0);
ial
STD_LOGIC_VECTOR (15
t STD_LOGIC_VECTOR (15
```

```
n, led => led_out);
```
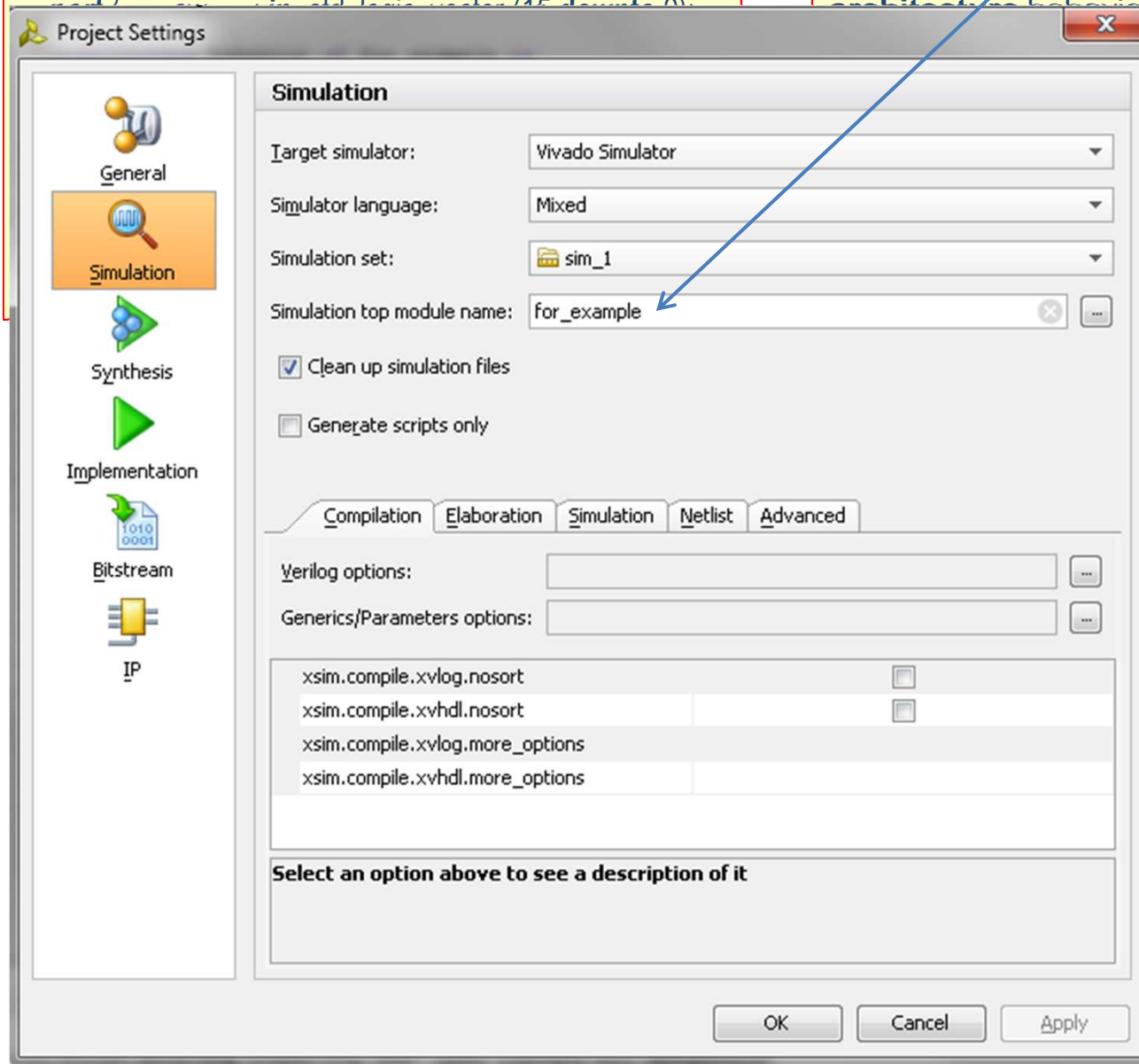
```
'1');
) ns;
'1');
00 ns;
o 10 => '1', others => '0');
) ns;
10101010";
) ns;
o 13 => '1', 10 => '1', 6 downto 5
```



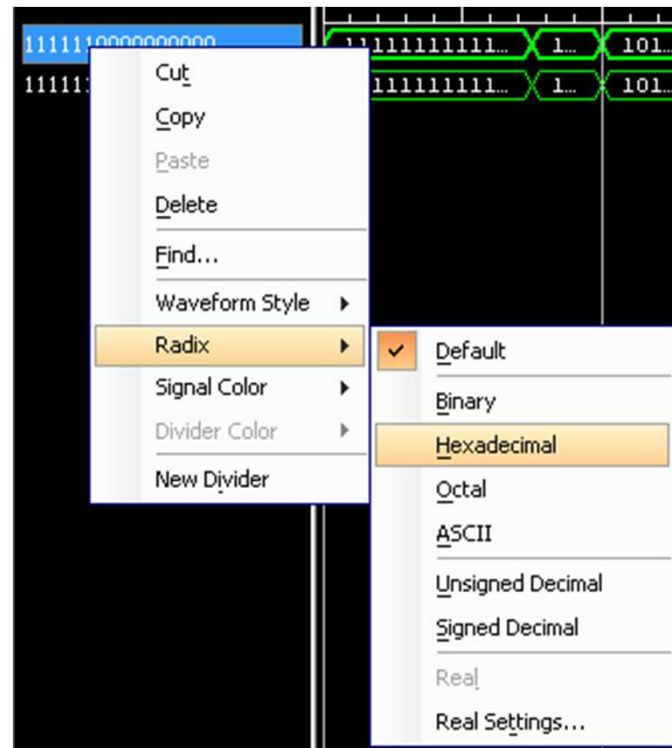 

 

```

library IEEE;
use IEEE.std_logic_1164.all;
entity for_example is
end for_example;
architecture behavior of for_example is
    signal sw_in    : std_logic_vector (15 downto 0);
    signal led_out   : std_logic_vector (15 downto 0);
    component TopTrivial
    port (   sw    : in  STD_LOGIC_VECTOR (15 downto 0);
           led    : out STD_LOGIC_VECTOR (15 downto 0));
    end component;
begin
    uut: TopTrivial
    port map (sw => sw_in, led => led_out);
    stim_proc: process
    begin
        sw_in <= (others => '1');
        sw_in <= (others => '1');
        sw_in <= (15 downto 10 => '1', others => '0');
        sw_in <= "1010101010101010";
        sw_in <= (15 downto 13 => '1', 10 => '1', 6 downto 5 => '1', others => '0');
    end process;
end behavior;

```

wait for 50 ns;  
wait for 100 ns;  
wait for 50 ns;  
wait for 70 ns;

Pode alterar o código da seguinte forma:

remover

```
library IEEE;
use IEEE.std_logic_1164.all;
library xil_defaultlib;
entity for_example is
end for_example;
architecture behavior of for_example is
    signal sw_in    : std_logic_vector (15 downto 0);
    signal led_out   : std_logic_vector (15 downto 0);
    component TopTrivial
    port (sw : in STD_LOGIC_VECTOR (15 downto 0);
         led : out STD_LOGIC_VECTOR (15 downto 0));
    end component;
begin
    uut: TopTrivial
    uut: entity xil_defaultlib.TopTrivial
    port map (sw => sw_in, led => led_out);
    stim_proc: process
    begin
        sw_in <= (others => '1');
        sw_in <= (others => '1');
        sw_in <= (15 downto 10 => '1', others => '0');
        sw_in <= "1010101010101010";
        sw_in <= (15 downto 13 => '1', 10 => '1', 6 downto 5 => '1', others => '0');
    end process;
end behavior;
```

```
wait for 50 ns;
wait for 100 ns;
wait for 50 ns;
wait for 70 ns;
```

## Simulação. Exemplo 2 (divisor da frequência).

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;

use IEEE.STD_LOGIC_UNSIGNED.all;
entity clock_divider is
port      ( clk, reset    : in std_logic;
            divided_clk : out std_logic      );
end clock_divider;
architecture Behavioral of clock_divider is
    signal internal_clock : std_logic_vector (2 downto 0);
begin
    process(clk)
    begin
        if rising_edge(clk) then
            if reset = '1' then      -- reset sincrono
                internal_clock <= (others=>'0');
            else
                internal_clock <= internal_clock+1;
            end if;
        end if;
    end process;
    divided_clk <= internal_clock(internal_clock'left);
end Behavioral;
```



```
library IEEE;
use IEEE.std_logic_1164.all;
library xil_defaultlib;
entity testbench is
end testbench;
architecture behavior of for_example is
    signal clk          : std_logic;
    signal rst          : std_logic;
    signal divided_clk   : std_logic;
    constant clk_period : time := 50 ns;
begin
    div: entity xil_defaultlib.clock_divider
    port map (clk, rst, divided_clk);
    clock_gen process
    begin
        clk <= '0';          wait for clk_period/2;
        clk <= '1';          wait for clk_period/2;
    end process clock_gen;
    stim_proc: process
    begin
        rst <= '1';          wait for 30 ns;
        rst <= '0';          wait for 1000 ns;
    end process;
end behavior;
```

50 us

**Run for 50us (Shift+F2)**  
Runs the simulation for the amount of time previously set with the 'Run For...' dialog.

30 us

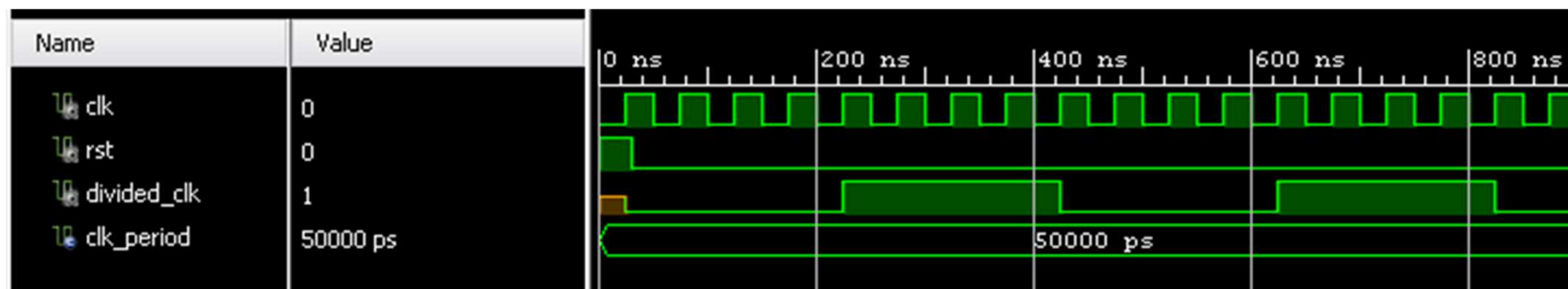 **Restart (Ctrl+Shift+F5)**  
Restarts the simulation from 'time 0'.





```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.numeric_std.all;
use IEEE.std_logic_unsigned.all;
entity Counter is
    port (reset      : in std_logic;
          clk        : in std_logic;
          My_count    : out std_logic_vector(3 downto 0));
end Counter;
architecture Behavioral of Counter is
    signal count : std_logic_vector(3 downto 0);
begin
    counter: process (clk)
    begin
        if rising_edge(clk) then
            if reset = '1' then
                count <= (others => '0');
            else
                count <= count + 1;
            end if;
        end if;
    end process counter;
    My_count <= count;
end Behavioral;


```

## Simulação. Exemplo 3 (contador).

```

library IEEE;
use IEEE.std_logic_1164.all;
library xil_defaultlib;
entity for_example is
end for_example;
architecture behavior of for_example is
    signal reset , clk : std_logic := '0';
    signal My_count : std_logic_vector(3 downto 0);
    constant clk_period : time := 50 ns;
begin
    uut: entity xil_defaultlib.Counter
    port map (clk, reset, My_count);
    clk_generator: process
    begin
        clk <= '0'; wait for clk_period/2;
        clk <= '1'; wait for clk_period/2;
    end process clk_generator;
    stim_proc: process
    begin
        reset <= '1';      wait for 50 ns;
        reset <= '0';      wait for 100 ns;
        reset <= '0';      wait for 100 ns;
        reset <= '0';      wait for 100 ns;
        reset <= '0';      wait for 500 ns;
    end process;
end behavior;

```

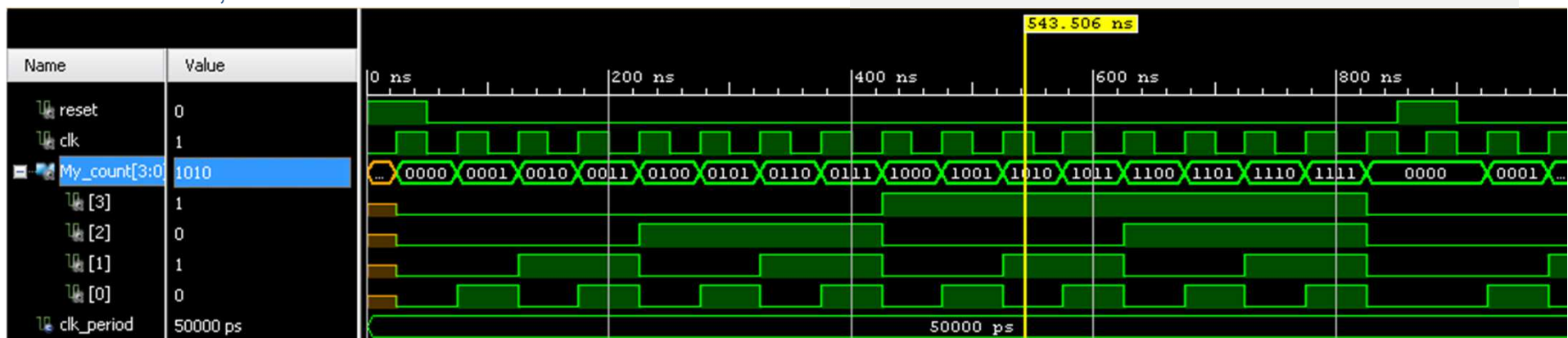

# Tipos de dados, objetos e operadores

Tipos

Vamos utilizar estes tipos:



Type	Where declared	Possible values
bit	standard in VHDL	'0', '1'
bit_vector	standard in VHDL	array of bits
boolean	standard in VHDL	false, true
character	standard in VHDL	7-bit ASCII codes in ISE
integer	standard in VHDL	at least 32 bits ( $-2^{31}$ to $2^{31}-1$ )
natural	standard in VHDL	subtype of integer: at least from 0 to $2^{31}-1$
positive	standard in VHDL	subtype of integer: at least from 1 to $2^{31}-1$
real	There are many restrictions for synthesis	floating-point values
signed	packages: ieee.std_logic_arith, array of std_logic ieee.numeric_std	
std_logic	package: ieee.std_logic_1164	resolved std_ulogic
std_logic_vector	package: ieee.std_logic_1164	array of std_logic
std_ulogic	package: ieee.std_logic_1164	'U', 'X', '0', '1', 'Z', 'W', 'L', 'H', '-'
std_ulogic_vector	package: ieee.std_logic_1164	array of std_ulogic
string	standard in VHDL	array of characters
time	standard in VHDL	time units: hr, min, sec, ms, us, ns, ps, fs
unsigned	packages: ieee.numeric_std, ieee.std_logic_arith	array of std_logic

Só para simulação

O tipo **record** é definido por utilizador e permite criar um conjunto de dados dentro de uma estrutura

# Tipos de dados, objetos e operadores

Vamos considerar três tipos de objetos que são:

1. Sinais (**signal**) que são declarados na parte declarativa de arquitetura.

```
architecture <nome de arquitetura > of <nome de entidade> is
  Declaração de sinais– signal
begin
    Corpo de arquitetura
end <nome de arquitetura >
```

2. Variáveis (**variable**) que são declaradas na parte declarativa de processo, função e procedimento.

```
process (sw)
  variable hwc : integer range 0 to 8;
begin
    -- .....
end process;
```

3. Constantes (**constant**) que são declaradas na parte declarativa de arquitetura, processo, função e procedimento.

```
architecture Behavioral of CombCircuit is
    type for_test is array (0 to 3) of std_logic_vector(3 downto 0);
    constant for_ex : for_test:=("0001","0010","0100","1000");
begin
    -- .....
```

# Tipos de dados, objetos e operadores

aritméticos (arithmetic)	(+, -, *, /, <b>abs</b> , <b>mod</b> , <b>rem</b> , sign + and -, **),
concatenação (concatenation)	(&),
lógicos (logic)	( <b>and</b> , <b>nand</b> , <b>nor</b> , <b>not</b> , <b>or</b> , <b>xnor</b> , <b>xor</b> ),
relacionais (relational)	(=, /=, <, <=, >, >=),
atribuição (assignment)	(:=, <=)
deslocamento (shift)	( <b>rol</b> , <b>ror</b> , <b>sla</b> , <b>sll</b> , <b>sra</b> , <b>srl</b> ).

## Prioridade (precedence) :

(\*\*),  
(**abs**),  
(**not**),  
(\*),  
(/),  
(**mod**, **rem**),  
(+ identity, - negation),  
(+, -),  
(&),  
(**rol**, **ror**, **sll**, **srl**),  
(**sla**, **sra**),  
(=, /=),  
(<, <=, >, >= ),  
(**and**, **nand**, **nor**, **or**, **xnor**, **xor**)

# Instruções de controlo – decisão: *if, when, with, case* .

## Processos combinatórios



Funcionamento

$SW_0$ $SW_1$	00	0001	{	$led_3$ $led_2$ $led_1$ $led_0$
	01	0010		
	10	0100		
	11	1000		

# Instruções de controlo – decisão: *if*, *when*, *with*, *case* .

## Processos combinatórios

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity CombCircuit is
    port ( sw      : in  std_logic_vector (1 downto 0);
          led      : out std_logic_vector (3 downto 0));
end CombCircuit;

architecture Behavioral of CombCircuit is
begin
    led <= "0001" when sw = "00" else
           "0010" when sw = "01" else
           "0100" when sw = "10" else
           "1000" when sw = "11" else "0000";

end Behavioral;
```

00	0001
01	0010
10	0100
11	1000

Utilizar dentro  
de arquitetura

# Instruções de controlo – decisão: *if*, *when*, *with*, *case* .

## Processos combinatórios

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity CombCircuit is
  port ( sw      : in  std_logic_vector (1 downto 0);
        led      : out std_logic_vector (3 downto 0));
end CombCircuit;

architecture Behavioral of CombCircuit is
begin
  with sw select led <=
    "0001" when "00",
    "0010" when "01",
    "0100" when "10",
    "1000" when "11",
    "0000" when others;

end Behavioral;
```

00	0001
01	0010
10	0100
11	1000

Utilizar dentro  
de arquitetura



# Instruções de controlo – decisão: *if*, *when*, *with*, *case* .

## Processos combinatórios

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity CombCircuit is
  port (  sw      : in  std_logic_vector (1 downto 0);
         led      : out std_logic_vector (3 downto 0));
end CombCircuit;
```

```
architecture Behavioral of CombCircuit is
begin
```

```
  process(sw)
  begin
    case sw is
      when "00" => led <= "0001";
      when "01" => led <= "0010";
      when "10" => led <= "0100";
      when "11" => led <= "1000";
      when others => led <= "0000";
    end case;
  end process;
```

```
end Behavioral;
```

00	0001
01	0010
10	0100
11	1000

Não pode (!!!)  
utilizar dentro  
de arquitetura

# Instruções de controlo – decisão: *if*, *when*, *with*, *case* .

## Processos combinatórios

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity CombCircuit is
  port (  sw      : in  std_logic_vector (1 downto 0);
         led      : out std_logic_vector (3 downto 0));
end CombCircuit;
```

```
architecture Behavioral of CombCircuit is
begin
```

```
process(sw)
begin
  if    sw = "00" then led <= "0001";
  elsif sw = "01" then led <= "0010";
  elsif sw = "10" then led <= "0100";
  elsif sw = "11" then led <= "1000";
  else   led <= "0000";
end if;
end process;
```

```
end Behavioral;
```

00	0001
01	0010
10	0100
11	1000

**Não pode (!!!)**  
utilizar dentro  
de arquitetura

## Utilização de constantes.

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;

entity CombCircuit is
    port ( sw      : in  std_logic_vector (1 downto 0);
          led      : out std_logic_vector (3 downto 0));
end CombCircuit;

architecture Behavioral of CombCircuit is
    type for_test is array (0 to 3) of std_logic_vector(3 downto 0);
    constant for_ex : for_test:=("0001","0010","0100","1000");
begin

    led <= for_ex(conv_integer(sw));

end Behavioral;
```

00	0001
01	0010
10	0100
11	1000

# Processos combinatórios

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;

entity TestCombProc is
port (    sw      : in  std_logic_vector(7 downto 0);
        led      : out std_logic_vector(7 downto 0));
end TestCombProc;

architecture Behavioral of TestCombProc is
    constant low      : integer := 5;
    constant high     : integer := 10;
begin

    process(sw)
    begin
        if (sw > low) and (sw < high) then led <= sw;
        elsif sw < low then led <= not sw;
        else led <= (others => '0');
        end if;
    end process;

end Behavioral;
```

led <= sw; para valores de interruptores 6,7,8,9 ("0110", "0111", "1000", "1001").

led <= **not** sw; para valores de interruptores 0, 1, 2, 3, 4.

Para outros valores de interruptores todos os leds são iguais a 0

*Todos os sinais que podem alterar valores dentro do processo devem aparecer na lista de sensibilidade*

## Processos sequenciais. Contador

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
use IEEE.STD_LOGIC_UNSIGNED.all;  
use IEEE.numeric_std.all;
```

```
entity TestSeqProc is  
generic ( how_fast : integer := 30);  
port (      clk      : in std_logic;  
        sw          : in  std_logic_vector(15 downto 0);  
  
        led         : out std_logic_vector(15 downto 0);  
        btnL        : in std_logic;  
        btnC        : in std_logic;  
        btnR        : in std_logic);  
end TestSeqProc;
```

```
architecture Behavioral of TestSeqProc is  
    signal internal_clock      : unsigned(how_fast downto 0);  
    signal divided_clk         : std_logic;  
    signal increment           : std_logic := btnL;  
    signal positive_reset      : std_logic := btnC;  
    signal count_enable        : std_logic := btnR;  
    signal count               : std_logic_vector(14 downto 0);  
begin
```

```
led(14 downto 0) <= count;  
led(15) <= divided_clk;
```

## Processos sequenciais. Contador

```
sp1: process(clk)
begin
  if rising_edge(clk) then      internal_clock <= internal_clock+1;
  end if;
  if falling_edge(clk) then
    divided_clk <= internal_clock(internal_clock'left - conv_integer(sw));
  end if;
end process sp1;
```

```
sp2: process (divided_clk)
begin
  if rising_edge(divided_clk) then
    if positive_reset = '1' then count <= (others=>'0');
    else
      if count_enable = '1' then
        if increment='0' then count <= count + 1;
        else count <= count - 1;
        end if;
      end if;
    end if;
  end if;
end process sp2;

end Behavioral;
```

## Processos sequenciais. Registo de deslocamento

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
use IEEE.STD_LOGIC_UNSIGNED.all;  
use IEEE.numeric_std.all;
```

```
entity TestSeqProc is  
generic ( how_fast : integer := 30);  
port (      clk      : in std_logic;  
        sw          : in  std_logic_vector(15 downto 0);  
        led         : out std_logic_vector(15 downto 0);  
        btnL        : in std_logic;  
        btnC        : in std_logic;  
        btnR        : in std_logic);  
end TestSeqProc;
```

```
architecture Behavioral of TestSeqProc is  
    signal internal_clock      : unsigned(how_fast downto 0);  
    signal divided_clk         : std_logic;  
    signal right               : std_logic := btnL;  
    signal positive_reset      : std_logic := btnC;  
    signal load_enable         : std_logic := btnR;  
    signal shift               : std_logic_vector(14 downto 0);  
begin
```

```
led(14 downto 0) <= shift;  
led(15) <= divided_clk;
```



## Processos sequenciais. Registo de deslocamento

```
sp1: process(clk)
begin
  if rising_edge(clk) then internal_clock <= internal_clock+1;
  end if;
  if falling_edge(clk) then
    divided_clk <= internal_clock(internal_clock'left);
  end if;
end process sp1;
```

```
sp3: process (divided_clk)
begin
  if rising_edge(divided_clk) then
    if positive_reset = '1' then shift <= (others=>'0');
    else
      if load_enable = '1' then shift <= sw;
      elsif right = '1' then
        shift <= shift(0) & shift(14 downto 1);
      else
        shift <= shift(13 downto 0) & shift(14);
      end if;
    end if;
  end if;
end process sp3;

end Behavioral;
```

# VHDL comportamental e estrutural


Descrição do comportamento semelhante à descrição na programação

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity behavioralVHDL is  
  port (x1, x2, x3 : in  std_logic;  
        y          : out std_logic);  
end BehavioralVHDL;
```

```
architecture behavioral of BehavioralVHDL is  
begin
```


```
  y <= (x1 and not x2 and not x3) or (not x1 and x2 and not x3) or (not x1 and not x2 and x3);
```

```
end behavioral;
```

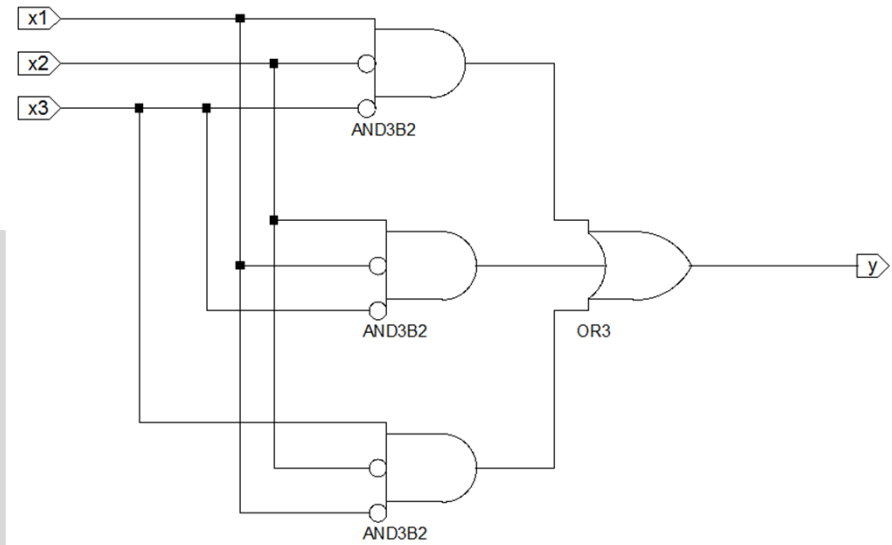
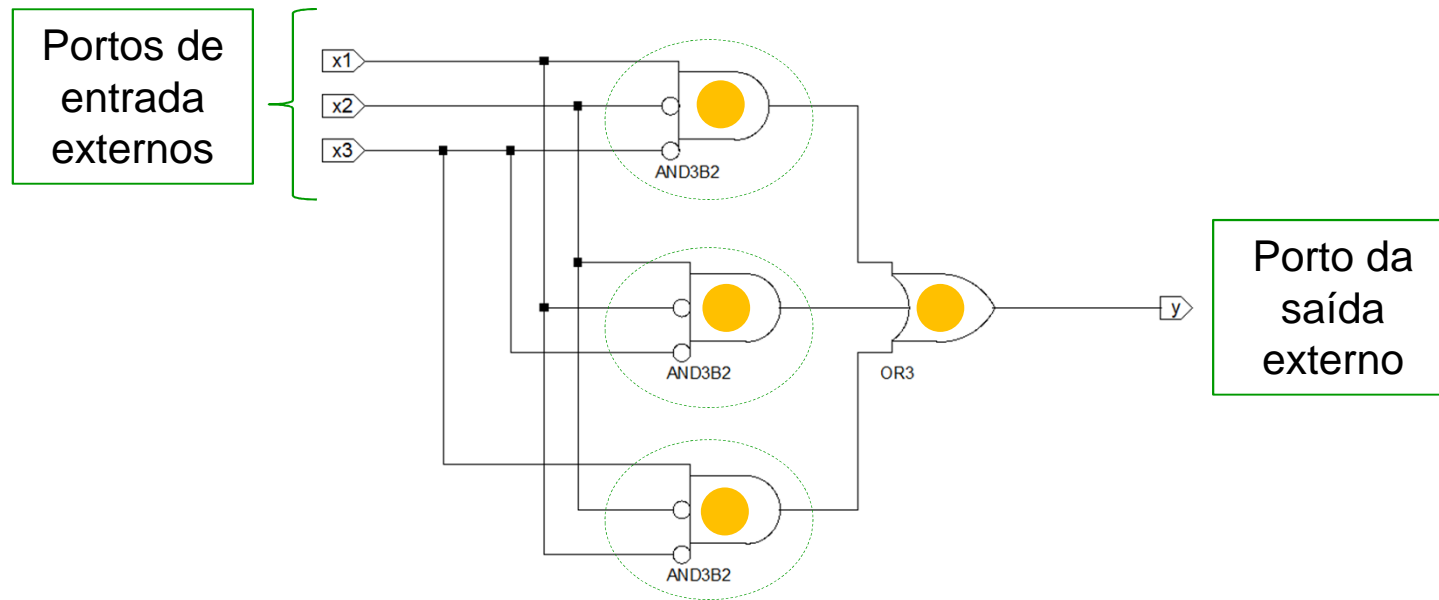
# VHDL comportamental e estrutural


Permite descrever um circuito com base em **componentes existentes** que são incluídos na descrição. Ligações entre componentes são escritas utilizando sinais



Biblioteca Xilinx UNISIM (ficheiro *unisim\_VCOMP.vhd*). Exemplo de descrição:

```
component AND3B3
  port (   O      : out      std_ulogic;
          I0, I1, I2 : in      std_ulogic);
end component;
```

# VHDL comportamental e estrutural

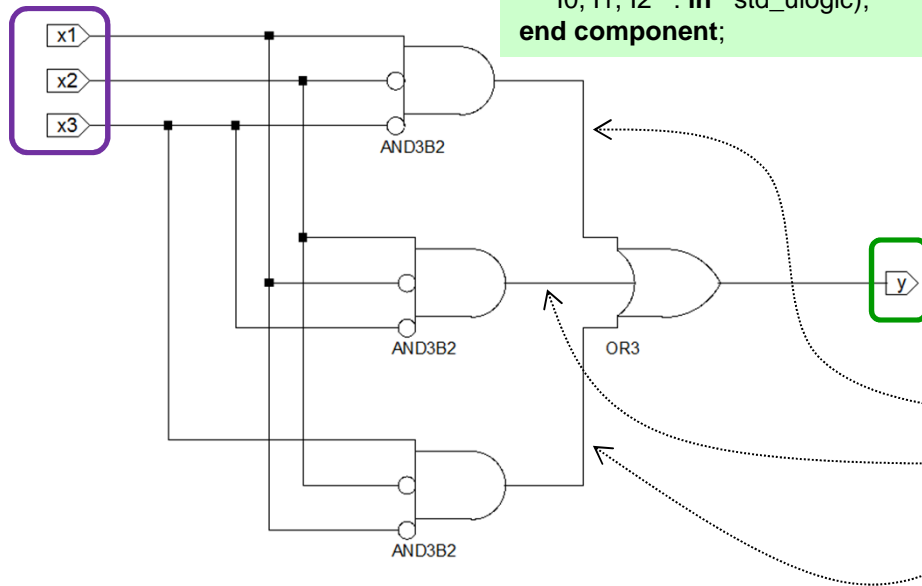

Mapeamento posicional

```
begin
  or_circuit : OR3
    port map (out_and1, out_and2, out_and3, y);

  and1_circuit : AND3B2
    port map (x3, x2, x1, out_and1);

  and2_circuit : AND3B2
    port map (x3, x1, x2, out_and2);

  and3_circuit : AND3B2
    port map (x1, x2, x3, out_and3);
end BEHAVIORAL;
```

```
library ieee;
use ieee.std_logic_1164.all;
```

```
library UNISIM;
use UNISIM.Vcomponents.all;
```

Biblioteca Xilinx

```
entity StructuralVHDL is
  port ( x1,x2,x3 : in std_logic;
         y       : out std_logic );
end StructuralVHDL;
```

architecture BEHAVIORAL of StructuralVHDL is

```
  signal out_and1 : std_logic;
  signal out_and2 : std_logic;
  signal out_and3 : std_logic;
begin
```

```
  or_circuit : OR3
    port map (I0=>out_and1, I1=>out_and2,
              I2=>out_and3, O=>y);
```

```
  and1_circuit : AND3B2
    port map (I0=>x3, I1=>x2, I2=>x1, O=>out_and1);
```

```
  and2_circuit : AND3B2
    port map (I0=>x3, I1=>x1, I2=>x2, O=>out_and2);
```


```
  and3_circuit : AND3B2
    port map (I0=>x1, I1=>x2, I2=>x3, O=>out_and3);
```

```
end BEHAVIORAL;
```

Mapeamento nomeado

# VHDL comportamental e estrutural

## Half-adder

 

```
library IEEE;
use IEEE.std_logic_1164.all;

entity half_adder is
    port ( A      : in std_logic;
          B      : in std_logic;
          carry_out : out std_logic;
          sum     : out std_logic);
end half_adder;



architecture half_adder_behavior of half_adder is
begin

    sum      <= A xor B;
    carry_out <= A and B;

end half_adder_behavior;
```

# VHDL comportamental e estrutural

## Half-adder (HA)

 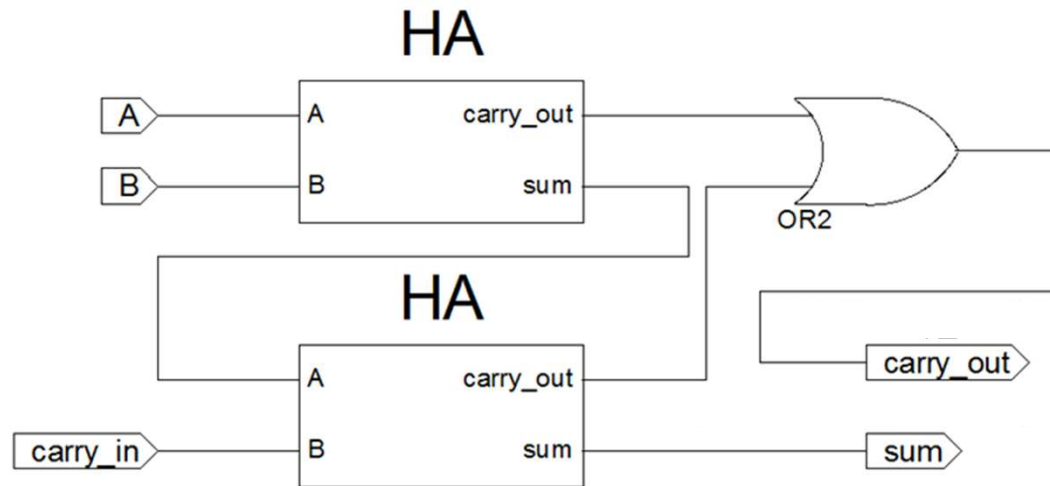

```

library IEEE;
use IEEE.std_logic_1164.all;
entity FULLADD is
port (      A, B, carry_in      : in  std_logic;
          sum, carry_out        : out std_logic );
end FULLADD;
architecture STRUCT of FULLADD is
    signal s1, s2, s3 : std_logic;
    component half_adder
    port(      A,B              : in  std_logic;
            carry_out, sum      : out std_logic);
    end component;
    begin
        u1: half_adder      port map(A, B, s2, s1);
        u2: half_adder      port map(s1, carry_in, s3, sum);
        carry_out <= s2 or s3;
    end STRUCT;
    
```

Descrição mista

```

library IEEE;
use IEEE.std_logic_1164.all;


entity half_adder is
    port (      A: in std_logic;
              B: in std_logic;
              carry_out : out std_logic;
              sum: out std_logic);
end half_adder;

architecture half_adder_behavior of
half_adder is
begin


    sum <= A xor B;
    carry_out <= A and B;

end half_adder_behavior;
    
```

# VHDL comportamental e estrutural

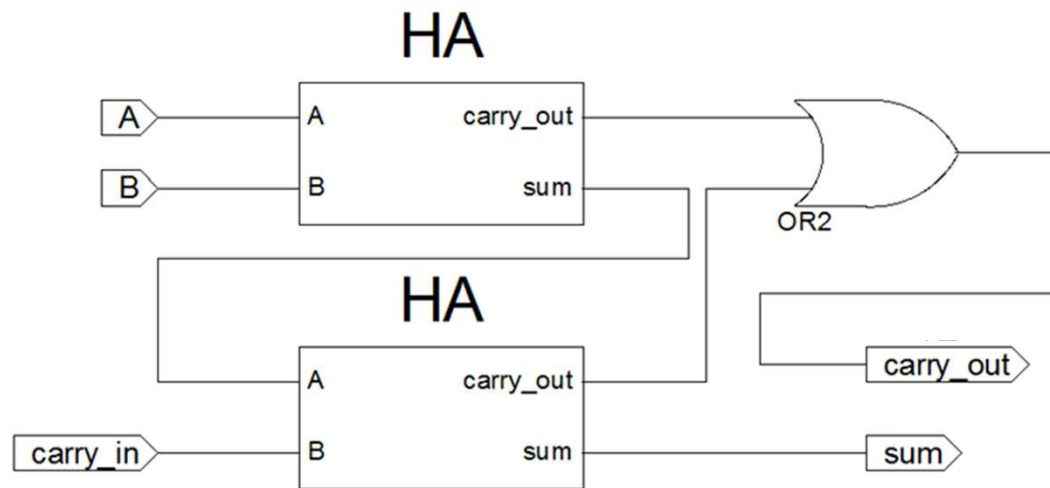

Half-adder (HA)

 

```
library IEEE;
use IEEE.std_logic_1164.all;

entity half_adder is
    port (
        A      : in std_logic;
        B      : in std_logic;
        carry_out : out std_logic;
        sum     : out std_logic;
    );
end half_adder;

architecture half_adder_behavior of half_adder is
begin
    sum <= A xor B;
    carry_out <= A and B;
end half_adder_behavior;
```

```
library IEEE;
use IEEE.std_logic_1164.all;
entity FULLADD is
    port (
        A, B, carry_in      : in std_logic;
        sum, carry_out      : out std_logic );
end FULLADD;
architecture STRUCT of FULLADD is
    signal s1, s2, s3 : std_logic;
    component half_adder
        port(
            A,B          : in std_logic;
            carry_out, sum : out std_logic);
    end component;
begin
    u1: half_adder      port map(A, B, s2, s1);
    u2: half_adder      port map(s1, carry_in, s3, sum);
    carry_out <= s2 or s3;
end STRUCT;
```


Descrição mista

library xil\_defaultlib;

entity xil\_defaultlib.half\_adder




# Exemplos: operações aritméticas

 

**Pode criar em Vivado um projeto com base em qualquer projeto existente**

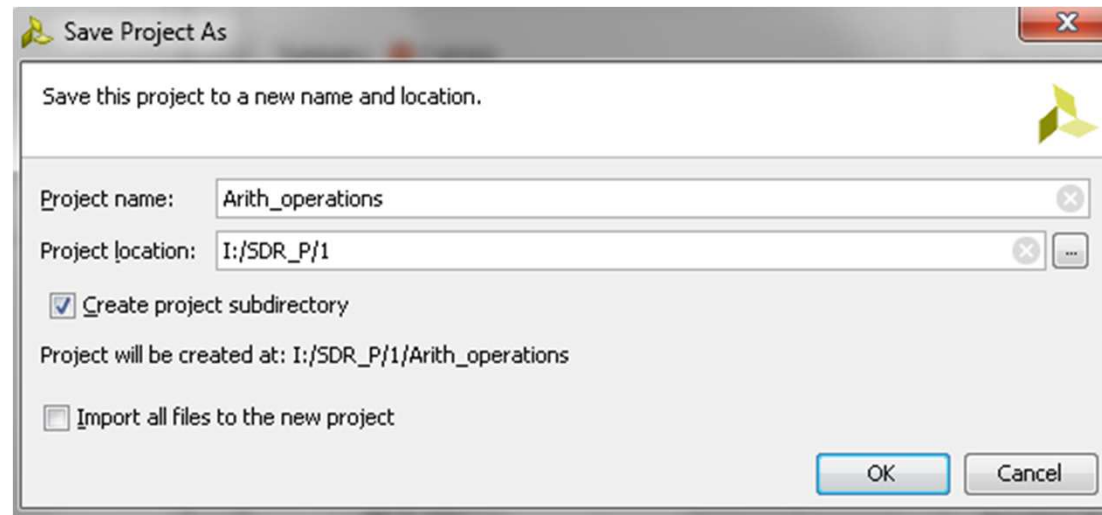**Depois pode só alterar código VHDL e modificar o ficheiro XDC**



## Exemplos: operações aritméticas

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.STD_LOGIC_ARITH.all;
entity arith_op is
port (      sw      : in std_logic_vector(7 downto 0);
        led         : out std_logic_vector(8 downto 0);
        btnU, btnC, btnD, btnL, btnR : in std_logic);
end arith_op;
-- btnR division; btnL multiplication; btnD addition; btnC subtraction; btnU rest of division
architecture Behavioral of arith_op is
    signal result      : integer range 0 to 256;
    signal but          : std_logic_vector(4 downto 0);
begin
    but <= btnU & btnC & btnD & btnL & btnR;
    result <= 256 when conv_integer(sw(3 downto 0)) = 0 else
        conv_integer(sw(7 downto 4)) / conv_integer(sw(3 downto 0))
        when but = "00001" else
        conv_integer(sw(7 downto 4)) * conv_integer(sw(3 downto 0))
        when but = "00010" else
        conv_integer(sw(7 downto 4)) + conv_integer(sw(3 downto 0))
        when but = "00100" else
        conv_integer(sw(7 downto 4)) - conv_integer(sw(3 downto 0))
        when but = "01000" else
        conv_integer(sw(7 downto 4)) rem conv_integer(sw(3 downto 0))
        when but = "10000" else 0;
    led(7 downto 0) <= conv_std_logic_vector(result, 8);
end Behavioral;
```

## Exemplos: operações aritméticas

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.numeric_std.all;      -- use IEEE.STD_LOGIC_ARITH.all;
entity arith_op is
port (      sw      : in std_logic_vector(7 downto 0);
      led         : out std_logic_vector(8 downto 0);
      btnU, btnC, btnD, btnL, btnR : in std_logic);
end arith_op;
-- btnR division; btnL multiplication; btnD addition; btnC subtraction; btnU rest of division
architecture Behavioral of arith_op is
    signal result      : integer range 0 to 256;
    signal but         : std_logic_vector(4 downto 0);
begin
    but <= btnU & btnC & btnD & btnL & btnR;
    result <= 256 when conv_integer(sw(3 downto 0)) = 0 else
        conv_integer(sw(7 downto 4)) / conv_integer(sw(3 downto 0))
        when but = "00001" else
        conv_integer(sw(7 downto 4)) * conv_integer(sw(3 downto 0))
        when but = "00010" else
        conv_integer(sw(7 downto 4)) + conv_integer(sw(3 downto 0))
        when but = "00100" else
        conv_integer(sw(7 downto 4)) - conv_integer(sw(3 downto 0))
        when but = "01000" else
        conv_integer(sw(7 downto 4)) rem conv_integer(sw(3 downto 0))
        when but = "10000" else 0;
    led(7 downto 0) <= std_logic_vector(to_unsigned(result,8)); --led(7 downto 0) <= conv_std_logic_vector(result, 8);
end Behavioral;
```

# Exemplos: processos

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.numeric_std.all;
entity arith_op is
port (      sw      : in std_logic_vector(7 downto 0);
      led      : out std_logic_vector(8 downto 0);
      btnU, btnC, btnD, btnL, btnR : in std_logic);
end arith_op;
-- btnR division; btnL multiplication; btnD addition; btnC subtraction; btnU rest of division
architecture Behavioral of arith_op is
  signal result : integer range 0 to 256;
  signal but : std_logic_vector(4 downto 0);
begin
  but <= btnU & btnC & btnD & btnL & btnR;
  process(but,sw)
  begin
    if conv_integer(sw(3 downto 0)) /= 0 then
      case but is
        when "00001" => result <= conv_integer(sw(7 downto 4)) / conv_integer(sw(3 downto 0));
        when "00010" => result <= conv_integer(sw(7 downto 4)) * conv_integer(sw(3 downto 0));
        when "00100" => result <= conv_integer(sw(7 downto 4)) + conv_integer(sw(3 downto 0));
        when "01000" => result <= conv_integer(sw(7 downto 4)) - conv_integer(sw(3 downto 0));
        when "10000" => result <= conv_integer(sw(7 downto 4)) rem conv_integer(sw(3 downto 0));
        when others => result <= 0;
      end case;
    else result <= 256;
    end if;
  end process;

  led(7 downto 0) <= std_logic_vector(to_unsigned(result,8));

end Behavioral;
```

## Processo combinatório

## Exemplos: conversão de tipos

```
signed_vector      <= signed(std_logic_vector_signal);
unsigned_vector    <= unsigned(std_logic_vector_signal);
std_logic_vector_signal <= std_logic_vector(signed_vector);
std_logic_vector_signal <= std_logic_vector(unsigned_vector);
```

Seguintes expressões devem utilizar funções de conversão:



```
integer_signal     <= conv_integer (unsigned_vector);
integer_signal     <= conv_integer (signed_vector);
integer_signal     <= conv_integer (std_logic_vector_signal);
unsigned_vector    <= conv_unsigned (integer_signal, size_of_unsigned_vector);
signed_vector      <= conv_signed (integer_signal, size_of_signed_vector);
std_logic_vector_signal <= conv_std_logic_vector (integer_signal, size);
```

As funções de conversão são diferentes para *pacotes diferentes*



```
use ieee.std_logic_arith.all; → led(7 downto 0) <= conv_std_logic_vector(result, 8);
```

```
use ieee.numeric_std.all;   → led(7 downto 0) <= std_logic_vector(to_unsigned(result,8));
```

 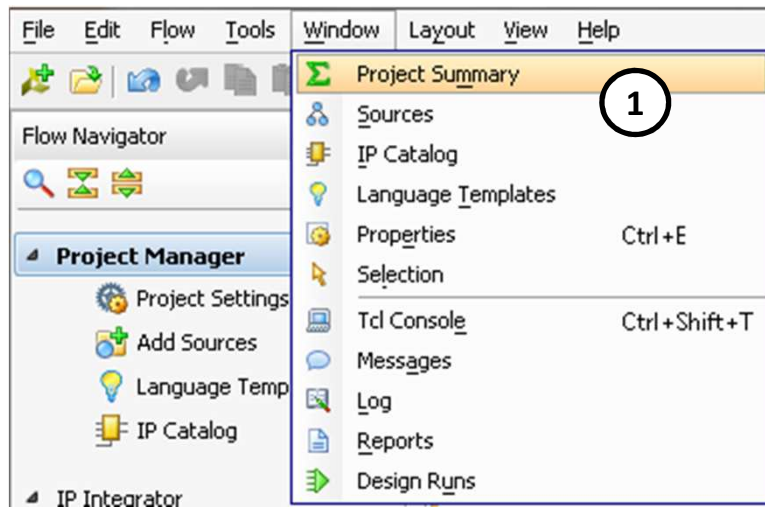
# Como encontrar recursos da FPGA utilizados para o seu projeto



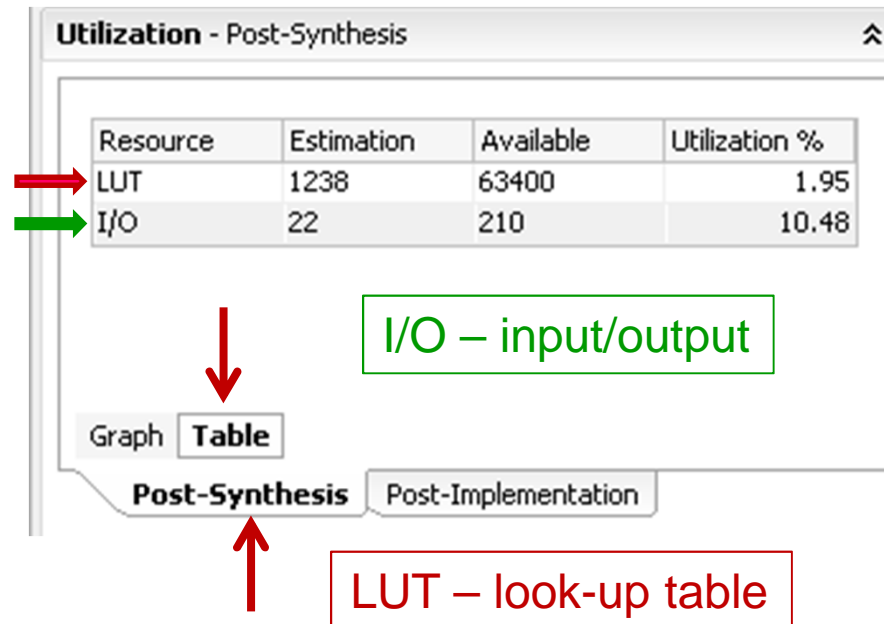 
1 CLB = 2 slices.  
1 slice = 4 LUTs e 8 flip-flops


 
## FPGA Artix-7 (família 7 de FPGAs de Xilinx)





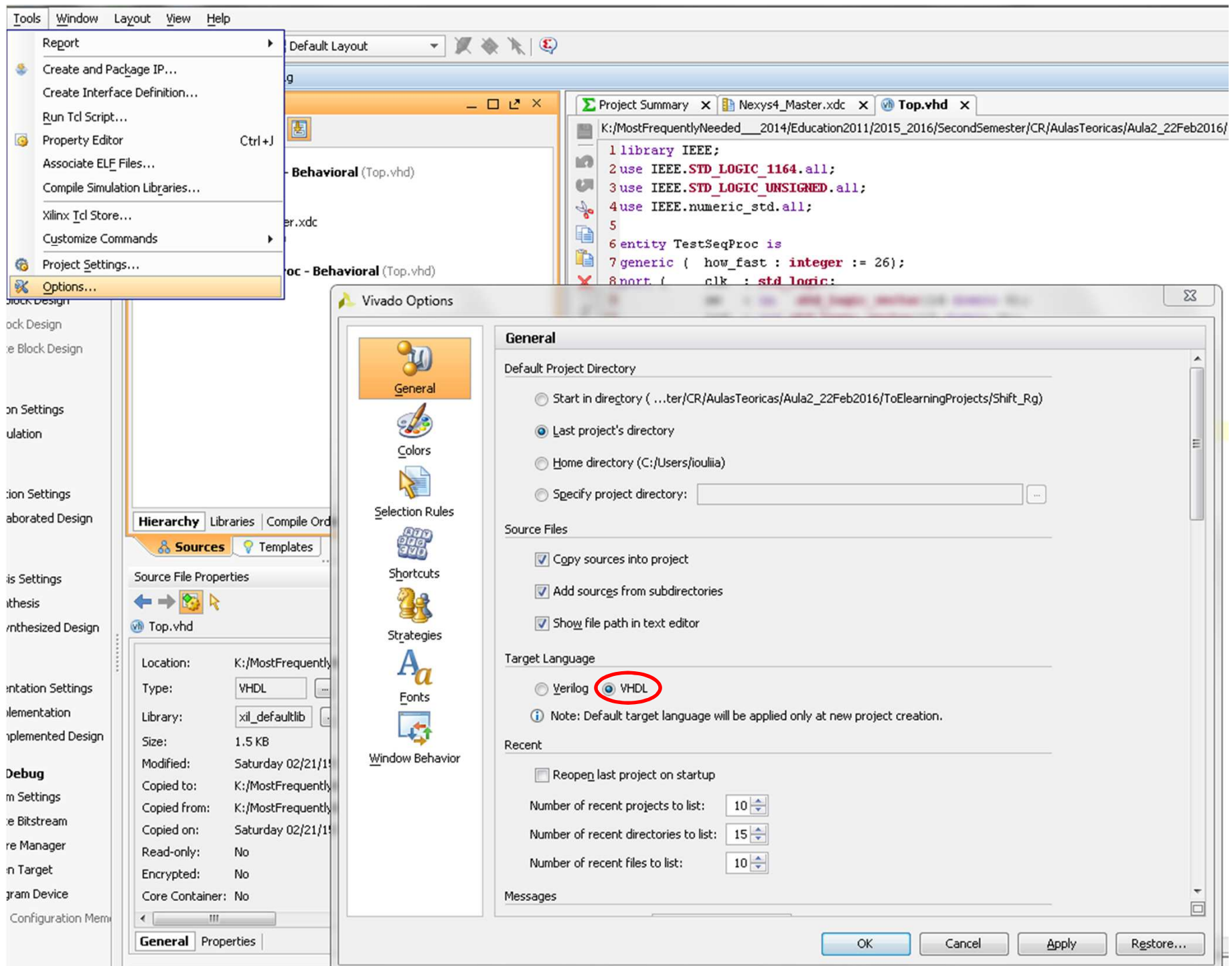



**New Project**

**Default Part**

Choose a default Xilinx part or board for your project. This can be changed later.

Select: ☒ Parts ☐ Boards

Filter

Product category: All Speed grade: -1

Family: Artix-7 Temp grade: C


Package: csg324

Reset All Filters

Search:

Part	I/O Pin Count	Block RAMs	DSPs	FlipFlops	GTPE2 Transceivers	Gb Transceivers	Available IOBs	LUT Elements
xc7a15tcsg324-1	324	25	45	20800	0	0	210	10400
xc7a35tcsg324-1	324	50	90	41600	0	0	210	20800
xc7a50tcsg324-1	324	75	120	65200	0	0	210	32600
xc7a75tcsg324-1	324	105	180	94400	0	0	210	47200
xc7a100tcsg324-1	324	135	240	126800	0	0	210	63400

< Back Next > Finish Cancel

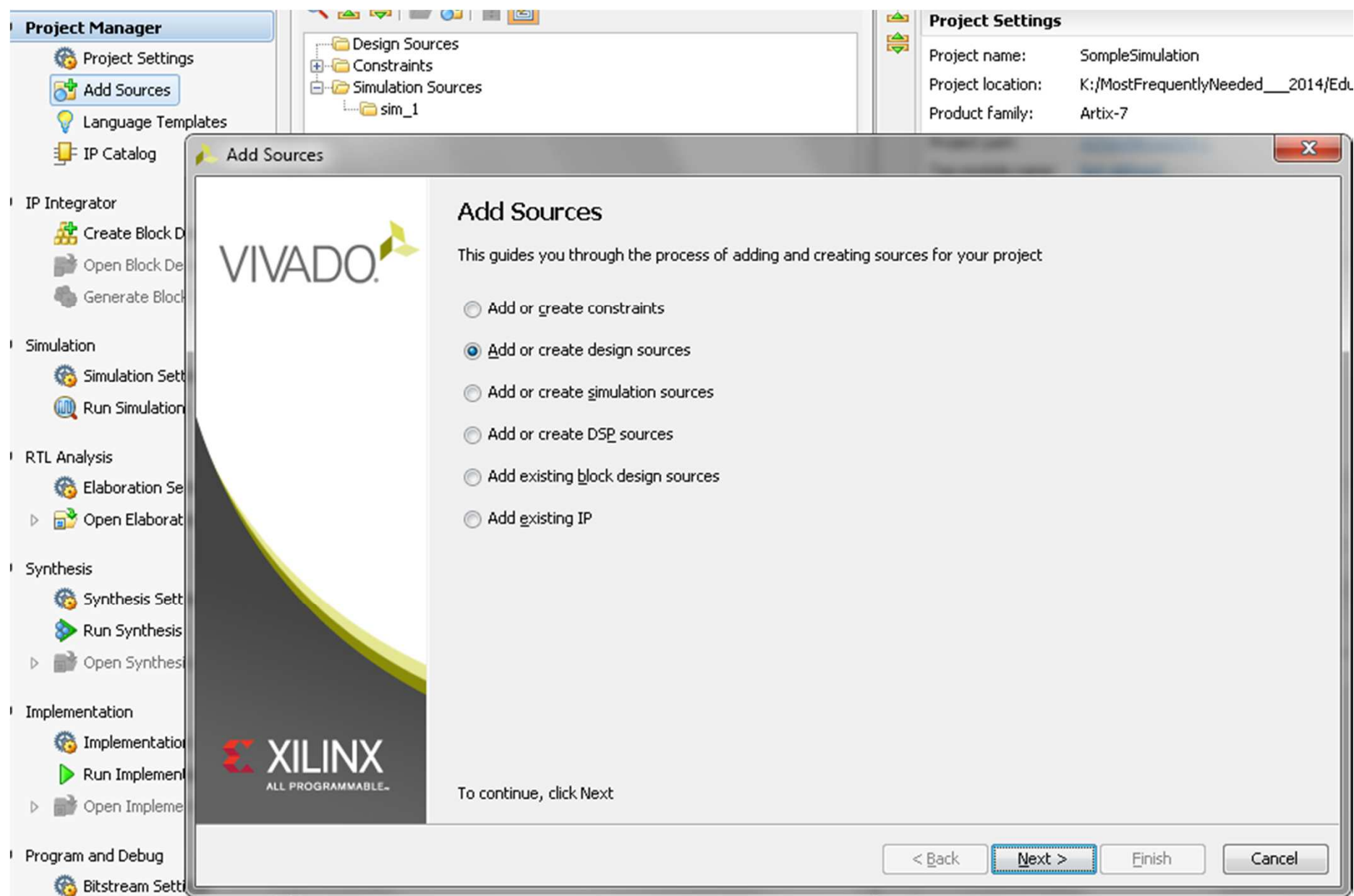

**Define Module**

Define a module and specify I/O Ports to add to your source file.  
 For each port specified:  
 MSB and LSB values will be ignored unless its Bus column is checked.  
 Ports with blank names will not be written.

Module Definition

Entity name:

Architecture name:

I/O Port Definitions

+	Port Name	Direction	Bus	MSB	LSB
—	sw	in	<input checked="" type="checkbox"/>	15	0
↑	led	out	<input checked="" type="checkbox"/>	15	0
↓		in	<input type="checkbox"/>		0

OK Cancel

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ForSim is
  Port ( sw : in STD_LOGIC_VECTOR (15 downto 0);
        led : out STD_LOGIC_VECTOR (15 downto 0));
end ForSim;

architecture Behavioral of ForSim is

begin


end Behavioral;
  
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ForSim is
    Port ( sw : in STD_LOGIC_VECTOR (15 downto 0);
          led : out STD_LOGIC_VECTOR (15 downto 0));
end ForSim;

architecture Behavioral of ForSim is

 begin
    led <= not sw;
end Behavioral;
```



```

library IEEE;
use IEEE.std_logic_1164.all;
library xil_defaultlib;
    entity for_example is
    end for_example;
architecture behavior of for_example is
    signal ssw : STD_LOGIC_VECTOR (15 downto 0);
    signal lled : STD_LOGIC_VECTOR (15 downto 0);
    -- constant clk_period      : time := 50 ns;
begin
    uut: entity xil_defaultlib.ForSim
        port map (sw=>ssw, led=>lled);
    --clk_generator: process
    --begin
    --  clk <= '0';      wait for clk_period/2;
    --  clk <= '1';      wait for clk_period/2;
    --end process clk_generator;
    stim_proc: process
    begin
        ssw <= "1111111100000000";      wait for 100 ns;
        ssw <= "0101010101010101";      wait for 100 ns;
    end process;

end behavior;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ForSim is
    Port ( sw : in STD_LOGIC_VECTOR (15 downto 0);
          led : out STD_LOGIC_VECTOR (15 downto 0));
end ForSim;

architecture Behavioral of ForSim is

begin
    led <= not sw;
end Behavioral;

```

## Behavioral Simulation - Functional - sim\_1 - for\_example

